

a)

```

module trap_edge(
    input logic async_sig, clk, reset,
    output logic trapped_edge);
    logic Q;
    always_ff @(posedge async_sig, posedge reset) begin
        if(reset) Q <= 1'b0;
        else Q <= 1'b1;
    end
    always_ff @(posedge clk, posedge reset) begin
        if(reset) trapped_edge <= 1'b0;
        else trapped_edge <= Q;
    end
end
endmodule


```

5/6

```

1 module trap_edge(
2     input logic async_sig, clk, reset,
3     output logic trapped_edge
4 );
5     logic Q;
6
7     always_ff @(posedge async_sig, posedge reset) begin
8         if(reset) Q <= 1'b0;
9         else Q <= 1'b1;
10    end
11
12    always_ff @(posedge clk, posedge reset) begin
13        if(reset) trapped_edge <= 1'b0;
14        else trapped_edge <= Q;
15    end
16
17 endmodule

```

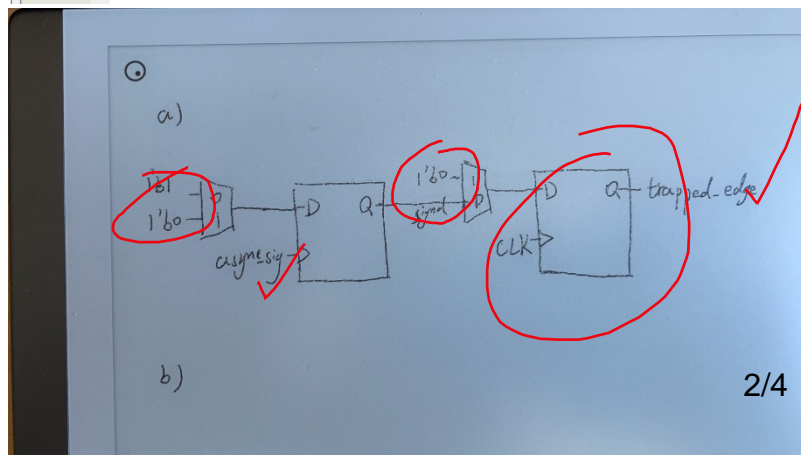

```

b)
module shared_access_to_one_state_machine
#(
parameter N = 32,
parameter M = 8
)
(

input target_state_machine_finished,
input sm_clk,
input logic start_request_a,
input logic start_request_b,
input [(N-1):0] input_arguments_a,
input [(N-1):0] input_arguments_b,
input reset,
input [M-1:0] in_received_data,

output logic finish_a,//
output logic finish_b,//
output logic reset_start_request_a,//
output logic reset_start_request_b,//
output reg [(M-1):0] received_data_a,
output reg [(M-1):0] received_data_b,
output reg [(N-1):0] output_arguments,
output start_target_state_machine//

);

logic [11:0] state;
parameter check_start_a =      12'b0000_00000000;
parameter give_start_a =      12'b0001_01100000;
parameter wait_for_finish_a = 12'b0010_00000000;
parameter register_data_a =   12'b0011_00000010;
parameter give_finish_a =     12'b0100_00001000;

parameter check_start_b =      12'b0101_10000000;
parameter give_start_b =      12'b0110_11010000;
parameter wait_for_finish_b = 12'b0111_10000000;
parameter register_data_b =   12'b1000_10000001;
parameter give_finish_b =     12'b1001_10000100;

logic          select_b_output_parameters,          register_data_a_enable,
register_data_b_enable;

```

```

//list the output with different state
assign register_data_b_enable = state[0];
assign register_data_a_enable = state[1];
assign finish_b = state[2];
assign finish_a = state[3];
assign reset_start_request_b = state[4];
assign reset_start_request_a = state[5];
assign start_target_state_machine = state[6];
assign select_b_output_parameters = state[7];

//select_b_output_parameters: the function of this state machine output is (in
pseudo-code):
assign output_arguments = (select_b_output_parameters) ? input_arguments_b :
input_arguments_a;

//register_data_a_enable & register_data_b_enable:
always_ff @(posedge sm_clk) begin
    if(register_data_a_enable) received_data_a <= in_received_data;
    if(register_data_b_enable) received_data_b <= in_received_data;
end

//state machine
always_ff @(posedge sm_clk, posedge reset)begin
    if(reset) state <= check_start_a;
    else
        case(state)

            check_start_a: begin
                if (!start_request_a) state <= check_start_b;
                else if (start_request_a) state <= give_start_a;
                else state <= check_start_a;
            end

            give_start_a: state <= wait_for_finish_a;

            wait_for_finish_a: begin
                if (!target_state_machine_finished) state <= wait_for_finish_a;
                else if (target_state_machine_finished) state <= register_data_a;
                else state <= wait_for_finish_a;
            end

            register_data_a: state <= give_finish_a;

            give_finish_a: state <= check_start_b;

```

```

check_start_b: begin
    if (!start_request_b) state <= check_start_a;
    else if (start_request_b) state <= give_start_b;
    else state <= check_start_b;
end

give_start_b: state <= wait_for_finish_b;

wait_for_finish_b: begin
    if (!target_state_machine_finished) state <= wait_for_finish_b;
    else if (target_state_machine_finished) state <= register_data_b;
    else state <= wait_for_finish_b;
end

register_data_b: state <= give_finish_b;

give_finish_b: state <= check_start_a;

default: state <= check_start_a;
endcase
end

endmodule

```

38/40

```


1 module shared_access_to_one_state_machine
2   #(
3     parameter N = 32,
4     parameter M = 8
5   )
6   (
7     input target_state_machine_finished,
8     input sm_clk,
9     input logic start_request_a,
10    input logic start_request_b,
11    input [(N-1):0] input_arguments_a,
12    input [(N-1):0] input_arguments_b,
13    input reset,
14    input [(M-1):0] in_received_data,
15    output logic finish_a, //
16    output logic finish_b, //
17    output logic reset_start_request_a, //
18    output logic reset_start_request_b, //
19    output reg [(M-1):0] received_data_a,
20    output reg [(M-1):0] received_data_b,
21    output reg [(N-1):0] output_arguments,
22    output start_target_state_machine //
23  );
24
25  logic [11:0] state;
26  parameter check_start_a = 12'b0000_00000000;
27  parameter give_start_a = 12'b0001_01100000;
28  parameter wait_for_finish_a = 12'b0010_00000000;
29  parameter register_data_a = 12'b0011_00000010;
30  parameter give_finish_a = 12'b0100_00001000;
31
32  parameter check_start_b = 12'b0101_10000000;
33  parameter give_start_b = 12'b0110_11010000;
34  parameter wait_for_finish_b = 12'b0111_10000000;
35  parameter register_data_b = 12'b1000_10000001;
36  parameter give_finish_b = 12'b1001_10000100;
37
38  logic select_b_output_parameters, register_data_a_enable, register_data_b_enable;
39
40  //list the output with different state
41  assign register_data_b_enable = state[0];
42  assign register_data_a_enable = state[1];
43

```

```


43 //list the output with different state
44 assign register_data_b_enable = state[0];
45 assign register_data_a_enable = state[1];
46 assign finish_b = state[2];
47 assign finish_a = state[3];
48 assign reset_start_request_b = state[4];
49 assign reset_start_request_a = state[5];
50 assign start_target_state_machine = state[6];
51 assign select_b_output_parameters = state[7];
52
53 //select_b_output_parameters: the function of this state machine output is (in pseudo-code):
54 assign output_arguments = (select_b_output_parameters) ? input_arguments_b : input_arguments_a;
55
56 //register_data_a_enable & register_data_b_enable:
57 always_ff @(posedge sm_clk) begin
58     if(register_data_a_enable) received_data_a <= in_received_data;
59     if(register_data_b_enable) received_data_b <= in_received_data;
60 end
61
62 //state machine
63 always_ff @(posedge sm_clk, posedge reset)begin
64     if(reset) state <= check_start_a;
65     else
66         case(state)
67         |
68             check_start_a: begin
69                 if (!start_request_a) state <= check_start_b;
70                 else if (start_request_a) state <= give_start_a;
71                 else state <= check_start_a;
72             end
73         |
74             give_start_a: state <= wait_for_finish_a;
75         |
76             wait_for_finish_a: begin
77                 if (!target_state_machine_finished) state <= wait_for_finish_a;
78                 else if (target_state_machine_finished) state <= register_data_a;
79                 else state <= wait_for_finish_a;
80             end
81         |
82             register_data_a: state <= give_finish_a;
83         |
84             give_finish_a: state <= check_start_b;
85         |
86             check_start_b: begin
87                 if (!start_request_b) state <= check_start_a;
88                 if (!start_request_b) state <= check_start_a;
89                 else if (start_request_b) state <= give_start_b;
90                 else state <= check_start_b;
91             end
92         |
93             give_start_b: state <= wait_for_finish_b;
94         |
95             wait_for_finish_b: begin
96                 if (!target_state_machine_finished) state <= wait_for_finish_b;
97                 else if (target_state_machine_finished) state <= register_data_b;
98                 else state <= wait_for_finish_b;
99             end
100         |
101             register_data_b: state <= give_finish_b;
102         |
103             give_finish_b: state <= check_start_a;
104         |
105             default: state <= check_start_a;
106         endcase
107     end
108 endmodule

```

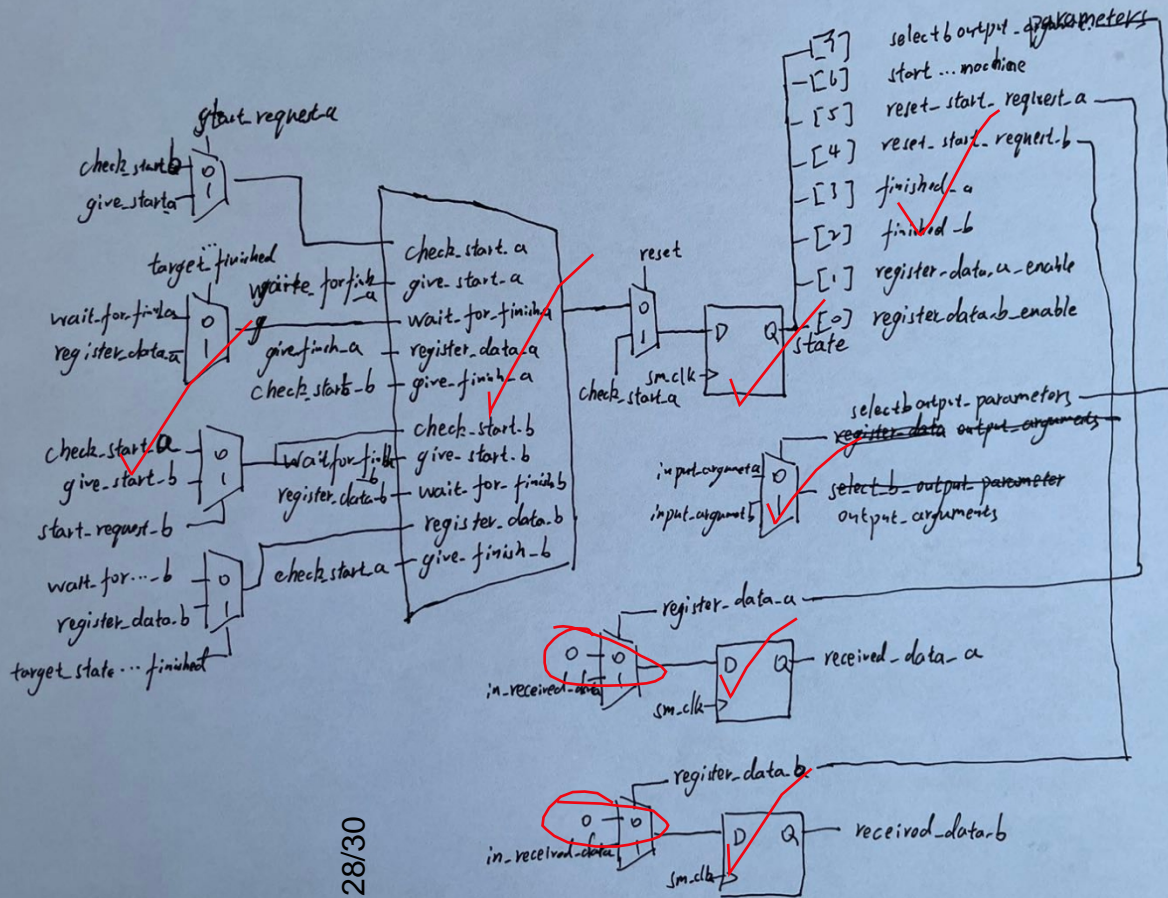

28/30

d)

 

when start\_request\_a is 1, the state change to give\_start\_a(0001/output:01100000)  
from check start a(0000/output:00000000)

```
then the state change to wait for finish a(0010/output:00000000)
```

when target\_state\_machine\_finished is 0, then the state change to wait for finish a(0010/output:00000000)

when target\_state\_machine\_finished is 1, then the state change to register data a(0011/output:00000010)

Then the state change to give\_finish\_a(0100/output:00001000), and check start b(0101/output:10000000)

when start\_request\_b is 1, the state change to give\_start\_b(0111/output:10000000)  
from check start b(0110/output:11010000)

then the state change to wait for finish b(0111/output:10000000)

when target\_state\_machine\_finished is 0, then the state change to wait for finish b(0111/output:10000000)

when target\_state\_machine\_finished is 1, then the state change to register data\_b(1000/output:10000001)

Then the state change to `give_finish_b(0101/output:10000100)`, and `check_start a(0000/output:00000000)`

If reset is 1, the state is check\_start\_a,

If (select\_b\_output\_parameters) = 1, output\_arguments = input\_arguments\_b, if (select\_b\_output\_parameters) = 0, output arguments = input arguments\_a

e)